

# 实验平台说明

特征	说明
操作系统版本和系统类型	Windows 7 64 bit enterprise edition
EDA 软件名称和版本	Quartus II 13.1 64 bit
DE2-115 开发板编号	1904615S

## 自查清单

特征	Part 7/Lab8	Part6/Lab8	Part/Lab	Part ?/Lab?
原理图	√	√	×	
Verilog 代码	√	√	×	
Flow Summary	√	√	×	
RTL 图	√	√	×	
状态机图	×	×	×	
工艺图	√	√	×	
仿真图	×	×	×	
SignalTapII 图	×	×	×	
硬件运行图	√	√	×	

## 第一部分 Part 7/Lab7

### 一、实验目的

1. 熟悉有限状态机的使用方法。
2. 联合数码管驱动电路进行状态设计。
3. 多个状态机串行使用。

### 二、实验内容

1. 使用 LAB1 中数码管驱动程序。
2. 使用 part1 中设计思路。
3. 以自己的方式设计驱动器。

### 三、实验原理

1. 以 SW0 开关为复位，以 KEY1 为 2 倍速按键，KEY2 为 2 倍慢速按键。
2. 输出映射到 8 个数码管上，进行流水灯 HELO 设计。

### 四、实验步骤

#### 1) 建立工程，并添加文件。

1. 建立工程，选择常用文件夹，取名为 lab3。
2. 添加 Block Diagram/Schematic 文件，取名为 lab3;
3. 添加 Verilog HDL 文件，取名为 PART4.5
4. 添加 VMF 文件，取名为 lab3.vmf

#### 2) 首先理清思路：

根据本实验所指导的方法来看，需要使用有限状态机来做 PART567，在 PART5 中首先是使用输入的 clk 进行 HELO 的流水

设计，涉及八个状态，所以使用一个三位的状态机指定不同的状态。在八个状态中，对八个状态进行内容设计：定义 HEX 状态，使除 hex0 外的每个 HEX 的数据往后流通。

### 3) 参考 PART56

在 PART7 中使用，三种状态可以使用两位的状态机进行状态调节，且由于状态比较少，所以也可绕过状态机，直接对状态进行调节。本实验使用第一种方案即传统 FSM。

### 4) 以 Verilog 代码表示。

### 5) 综合


Flow Summary	
Flow Status	Successful - Tue Dec 03 13:07:07 2019
Quartus II 64-Bit Version	13.1.0 Build 162 10/23/2013 SJ Full Version
Revision Name	LAB7
Top-level Entity Name	part7
Family	Cyclone IV E
Device	EP4CE115F29C7
Timing Models	Final
Total logic elements	140 / 114,480 ( < 1 % )
Total combinational functions	134 / 114,480 ( < 1 % )
Dedicated logic registers	80 / 114,480 ( < 1 % )
Total registers	80
Total pins	60 / 529 ( 11 % )
Total virtual pins	0
Total memory bits	0 / 3,981,312 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 532 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

### 6) 编译并将引脚对应。

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved (n)
HEX0[6]	Output	PIN_H22	6	B6_N0	PIN_H22	2.5 V (default)	
HEX0[5]	Output	PIN_J22	6	B6_N0	PIN_J22	2.5 V (default)	
HEX0[4]	Output	PIN_L25	6	B6_N1	PIN_L25	2.5 V (default)	
HEX0[3]	Output	PIN_L26	6	B6_N1	PIN_L26	2.5 V (default)	
HEX0[2]	Output	PIN_E17	7	B7_N2	PIN_E17	2.5 V (default)	8m
HEX0[1]	Output	PIN_F22	7	B7_N0	PIN_F22	2.5 V (default)	8m
HEX0[0]	Output	PIN_G18	7	B7_N2	PIN_G18	2.5 V (default)	8m
HEX1[6]	Output	PIN_U24	5	B5_N0	PIN_U24	2.5 V (default)	8m
HEX1[5]	Output	PIN_U23	5	B5_N1	PIN_U23	2.5 V (default)	8m
HEX1[4]	Output	PIN_W25	5	B5_N1	PIN_W25	2.5 V (default)	8m
HEX1[3]	Output	PIN_W22	5	B5_N0	PIN_W22	2.5 V (default)	8m
HEX1[2]	Output	PIN_W21	5	B5_N1	PIN_W21	2.5 V (default)	8m
HEX1[1]	Output	PIN_Y22	5	B5_N0	PIN_Y22	2.5 V (default)	8m
HEX1[0]	Output	PIN_M24	6	B6_N2	PIN_M24	2.5 V (default)	8m
HEX2[6]	Output	PIN_W28	5	B5_N1	PIN_W28	2.5 V (default)	8m
HEX2[5]	Output	PIN_W27	5	B5_N1	PIN_W27	2.5 V (default)	8m
HEX2[4]	Output	PIN_Y26	5	B5_N1	PIN_Y26	2.5 V (default)	8m
HEX2[3]	Output	PIN_W26	5	B5_N1	PIN_W26	2.5 V (default)	8m
HEX2[2]	Output	PIN_Y25	5	B5_N1	PIN_Y25	2.5 V (default)	8m
HEX2[1]	Output	PIN_AA26	5	B5_N1	PIN_AA26	2.5 V (default)	8m
HEX2[0]	Output	PIN_AA25	5	B5_N1	PIN_AA25	2.5 V (default)	8m
HEX3[6]	Output	PIN_Y19	4	B4_N0	PIN_Y19	2.5 V (default)	8m
HEX3[5]	Output	PIN_AF23	4	B4_N0	PIN_AF23	2.5 V (default)	8m
HEX3[4]	Output	PIN_AD24	4	B4_N0	PIN_AD24	2.5 V (default)	8m
HEX3[3]	Output	PIN_AA21	4	B4_N0	PIN_AA21	2.5 V (default)	8m
HEX3[2]	Output	PIN_AB20	4	B4_N0	PIN_AB20	2.5 V (default)	8m
HEX3[1]	Output	PIN_U21	5	B5_N0	PIN_U21	2.5 V (default)	8m

HEX3[0]	Output	PIN_V21	5	B5_N1	PIN_V21	2.5 V (default)	8m
HEX4[6]	Output	PIN_AE18	4	B4_N2	PIN_AE18	2.5 V (default)	8m
HEX4[5]	Output	PIN_AF19	4	B4_N1	PIN_AF19	2.5 V (default)	8m
HEX4[4]	Output	PIN_AE19	4	B4_N1	PIN_AE19	2.5 V (default)	8m
HEX4[3]	Output	PIN_AH21	4	B4_N2	PIN_AH21	2.5 V (default)	8m
HEX4[2]	Output	PIN_AG21	4	B4_N2	PIN_AG21	2.5 V (default)	8m
HEX4[1]	Output	PIN_AA19	4	B4_N0	PIN_AA19	2.5 V (default)	8m
HEX4[0]	Output	PIN_AB19	4	B4_N0	PIN_AB19	2.5 V (default)	8m
HEX5[6]	Output	PIN_AH18	4	B4_N2	PIN_AH18	2.5 V (default)	8m
HEX5[5]	Output	PIN_AF18	4	B4_N1	PIN_AF18	2.5 V (default)	8m
HEX5[4]	Output	PIN_AG19	4	B4_N2	PIN_AG19	2.5 V (default)	8m
HEX5[3]	Output	PIN_AH19	4	B4_N2	PIN_AH19	2.5 V (default)	8m
HEX5[2]	Output	PIN_AB18	4	B4_N0	PIN_AB18	2.5 V (default)	8m
HEX5[1]	Output	PIN_AC18	4	B4_N1	PIN_AC18	2.5 V (default)	8m
HEX5[0]	Output	PIN_AD18	4	B4_N1	PIN_AD18	2.5 V (default)	8m
HEX6[6]	Output	PIN_AC17	4	B4_N2	PIN_AC17	2.5 V (default)	8m
HEX6[5]	Output	PIN_AA15	4	B4_N2	PIN_AA15	2.5 V (default)	8m
HEX6[4]	Output	PIN_AB15	4	B4_N2	PIN_AB15	2.5 V (default)	8m
HEX6[3]	Output	PIN_AB17	4	B4_N1	PIN_AB17	2.5 V (default)	8m
HEX6[2]	Output	PIN_AA16	4	B4_N2	PIN_AA16	2.5 V (default)	8m
HEX6[1]	Output	PIN_AB16	4	B4_N2	PIN_AB16	2.5 V (default)	8m
HEX6[0]	Output	PIN_AA17	4	B4_N1	PIN_AA17	2.5 V (default)	8m
HEX7[6]	Output	PIN_AA14	3	B3_N0	PIN_AA14	2.5 V (default)	8m
HEX7[5]	Output	PIN_AG18	4	B4_N2	PIN_AG18	2.5 V (default)	8m
HEX7[4]	Output	PIN_AF17	4	B4_N2	PIN_AF17	2.5 V (default)	8m
HEX7[3]	Output	PIN_AH17	4	B4_N2	PIN_AH17	2.5 V (default)	8m
HEX7[2]	Output	PIN_AG17	4	B4_N2	PIN_AG17	2.5 V (default)	8m
HEX7[1]	Output	PIN_AE17	4	B4_N2	PIN_AE17	2.5 V (default)	8m
HEX7[0]	Output	PIN_AD17	4	B4_N2	PIN_AD17	2.5 V (default)	8m
KEY0	Input	PIN_M23	6	B6_N2	PIN_M23	2.5 V (default)	8m
KEY1	Input	PIN_M21	6	B6_N1	PIN_M21	2.5 V (default)	8m
SW[15]	Input	PIN_AA22	5	B5_N2	PIN_AA22	2.5 V (default)	8m
SW[14]	Input	PIN_AA23	5	B5_N2	PIN_AA23	2.5 V (default)	8m
SW[13]	Input	PIN_AA24	5	B5_N2	PIN_AA24	2.5 V (default)	8m
SW[12]	Input	PIN_AB23	5	B5_N2	PIN_AB23	2.5 V (default)	8m
SW[11]	Input	PIN_AB24	5	B5_N2	PIN_AB24	2.5 V (default)	8m
SW[10]	Input	PIN_AC24	5	B5_N2	PIN_AC24	2.5 V (default)	8m
SW[9]	Input	PIN_AB25	5	B5_N1	PIN_AB25	2.5 V (default)	8m
SW[8]	Input	PIN_AC25	5	B5_N2	PIN_AC25	2.5 V (default)	8m
SW[7]	Input	PIN_AB26	5	B5_N1	PIN_AB26	2.5 V (default)	8m
SW[6]	Input	PIN_AD26	5	B5_N2	PIN_AD26	2.5 V (default)	8m
SW[5]	Input	PIN_AC26	5	B5_N2	PIN_AC26	2.5 V (default)	8m
SW[4]	Input	PIN_AB27	5	B5_N1	PIN_AB27	2.5 V (default)	8m
SW[3]	Input	PIN_AD27	5	B5_N2	PIN_AD27	2.5 V (default)	8m
SW[2]	Input	PIN_AC27	5	B5_N2	PIN_AC27	2.5 V (default)	8m
SW[1]	Input	PIN_AC28	5	B5_N2	PIN_AC28	2.5 V (default)	8m
SW[0]	Input	PIN_AB28	5	B5_N1	PIN_AB28	2.5 V (default)	8m
KEY2	Unknown	PIN_N21	6	B6_N2		2.5 V (default)	8m

## 7) RTL 级视图

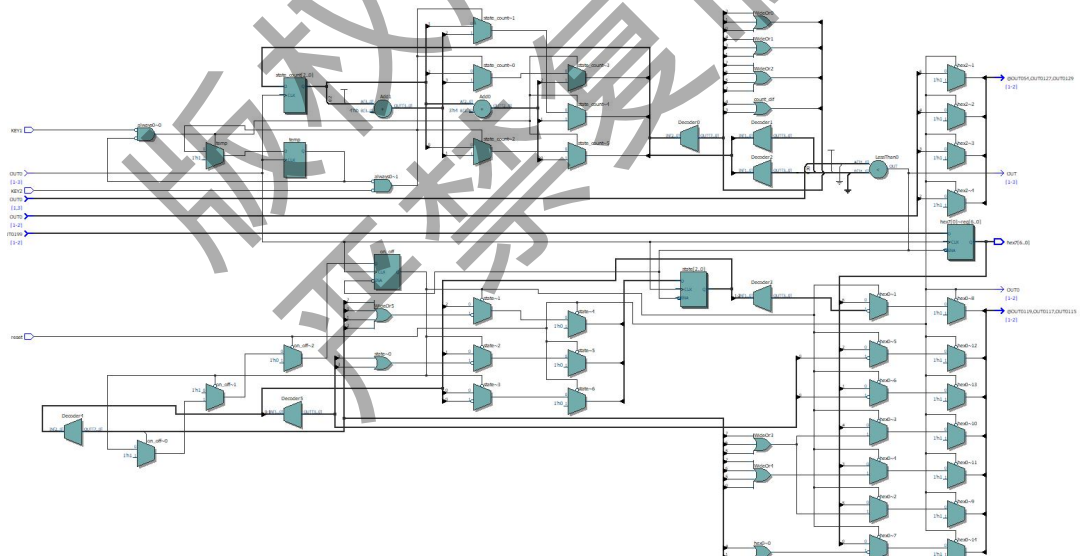

## 五、实验代码

```

module part7(hex7,hex6,hex5,hex4,hex3,
             hex2,hex1,hex0,clk,reset,KEY1,KEY2);

    output reg [6:0] hex7,hex6,hex5,hex4,hex3,hex2,hex1,hex0;

    input clk,reset,KEY1,KEY2;

```

```
reg [2:0] state;  
reg on_off;  
reg [2:0]state_count;  
reg temp;  
integer count;  
integer count_dif;
```

```
always @(posedge clk)  
begin//KEY1:clk=12500000 KEY2:clk=200000000  
if(KEY1==0&&temp==0)begin  
state_count=state_count+3'b001 ;temp=1;end  
else if(KEY2==0&&temp==0)begin  
state_count=state_count-3'b001 ;temp=1;end  
if(KEY1!=0&&KEY2!=0) begin temp=0; end  
begin  
case(state_count)  
3'b000:count_dif=12500000;  
3'b001:count_dif=25000000;  
3'b010:count_dif=50000000;  
3'b011:count_dif=100000000;  
3'b100:count_dif=200000000;
```

```
        default: count_dif=50000000;

endcase

end

if(count<count_dif)

    count=count+1;

else

begin

    begin

        if(reset==0)

            begin hex7<=7'b1111111;

                hex6<=7'b1111111;

                hex5<=7'b1111111;

                hex4<=7'b1111111;

                hex3<=7'b1111111;

                hex2<=7'b1111111;

                hex1<=7'b1111111;

                hex0<=7'b1111111;

                state<=3'b000;

                on_off=1'b0;

            end

        else
```

```

begin

//solve the first problem

    if(on_off==0)//at the beginning,set the register

        begin

            case(state)

                3'd0:begin

hex0<=7'b0001001;hex1<=hex0;hex2<=hex1;hex3<=hex2;

                hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;
end //H

                3'd1:begin

hex0<=7'b0000110;hex1<=hex0;hex2<=hex1;hex3<=hex2;

                hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;
end //E

                3'd2:begin

hex0<=7'b1000111;hex1<=hex0;hex2<=hex1;hex3<=hex2;

                hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;
end //L

                3'd3:begin

hex0<=7'b1000111;hex1<=hex0;hex2<=hex1;hex3<=hex2;

```

```
    hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;  
end    //L
```

```
    3'd4:begin
```

```
    hex0<=7'b1000000;hex1<=hex0;hex2<=hex1;hex3<=hex2;
```

```
    hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;  
end    //O
```

```
    3'd5:begin
```

```
    hex0<=7'b1111111;hex1<=hex0;hex2<=hex1;hex3<=hex2;
```

```
    hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;  
end
```

```
    3'd6:begin
```

```
    hex0<=7'b1111111;hex1<=hex0;hex2<=hex1;hex3<=hex2;
```

```
    hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;  
end
```

```
    3'd7:begin
```

```
    hex0<=7'b1111111;hex1<=hex0;hex2<=hex1;hex3<=hex2;
```

```
    hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;state=state+1;
```



```
on_off=1'b1;end
```

```
endcase
```

```
end
```

```
else
```

```
begin
```

```
hex0<=hex7;hex1<=hex0;hex2<=hex1;hex3<=hex2;
```

```
hex4<=hex3;hex5<=hex4;hex6<=hex5;hex7<=hex6;
```

```
end
```

```
end
```

```
end
```

```
count=0;
```

```
end
```


```
end
```

```
endmodule
```

## 六 实验体会

状态机十分好用，期末大作业可以用上的。



 

版权所有  
严禁复制